




founded by Philips




**Strategies and Devices for Cell Balancing**

**Joop van Lammeren**



**Outline**


- ▶ Why cell balancing
- ▶ How to balance cells
- ▶ Pros and cons


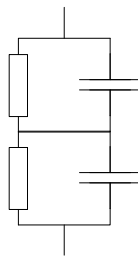
## Why cell balancing?




- ▶ Super-simple model
- ▶ Reality: non-linear, time-variant, temperature-dependent


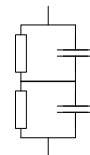
## Causes of cell unbalance



- ▶ Self discharge
  - increases with age, cycles, and temperature
- ▶ Capacity loss
  - increases with age, cycles, and temperature
  
- ▶ Charging process itself produces heat, not cell unbalance
  - Coulombic efficiency of a Lilon cell >99.9%
  - power efficiency of charging process is 70-95%



## Balancing and redistribution



- ▶ Self-discharge mismatch compensation
  - can be done while driving
  - bad cell will leak up to 10mA
  - required balance current level: up to 100mA
- ▶ Capacity mismatch compensation
  - must be done while driving
  - capacity mismatch can go up to 10%
  - traction motor can draw tens of amps
  - required redistribution current level: 1A and up



## Balancing vs redistribution




- ▶ Balancing
  - prevents range-decrease-over-time of the vehicle
  - all cells are full at the end of charging
  - 99 cells @ C = 100%, 1 cell @ C = 90% --> range = 90%
  - $Q_{bat} = N * Q_{worstcell} @ bestcellf \ddagger$
- ▶ Redistribution
  - maximises the range of the vehicle
  - all cells are full at the end of charging and empty at the end of discharging
  - 99 cells @ Q = 100%, 1 cell @ Q = 90% --> range = 99.9%
  - $C_{bat} = \sum_{i=1}^N C_i$


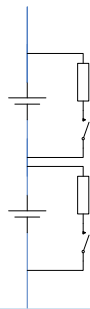
## Resistive balancing




- ▶ At rest: up to 100mA to bleed all cells except lowest-charged one
- ▶ During charging: several amps to bypass charge current of full cells


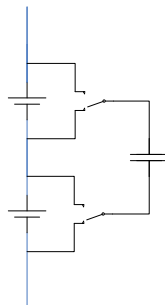
## Capacitive balancing




- ▶ Equivalent cell capacitance:  $\sim 1\text{MF}$
- ▶ Series resistances of cells and switches:  $\sim 0.1\Omega$
- ▶ Time-constant  $\sim 1$  day


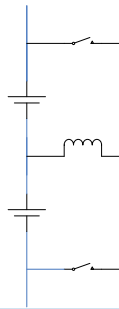
## Inductive balancing/redistribution




- ▶ Energy ripples through cells from source to destination
  - reduces efficiency and speed


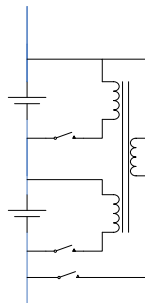
## Transformer balancing/redistribution



- ▶ Energy can be moved direct from source to destination



## Balancing approaches: pros and cons



- ▶ Resistive
  - no efficiency
  - simple, fast
- ▶ Capacitive
  - very slow
  - simple, high efficiency, no measurement necessary
- ▶ Inductive
  - cost
  - high efficiency, fast
- ▶ Transformer
  - cost
  - high efficiency, fast

